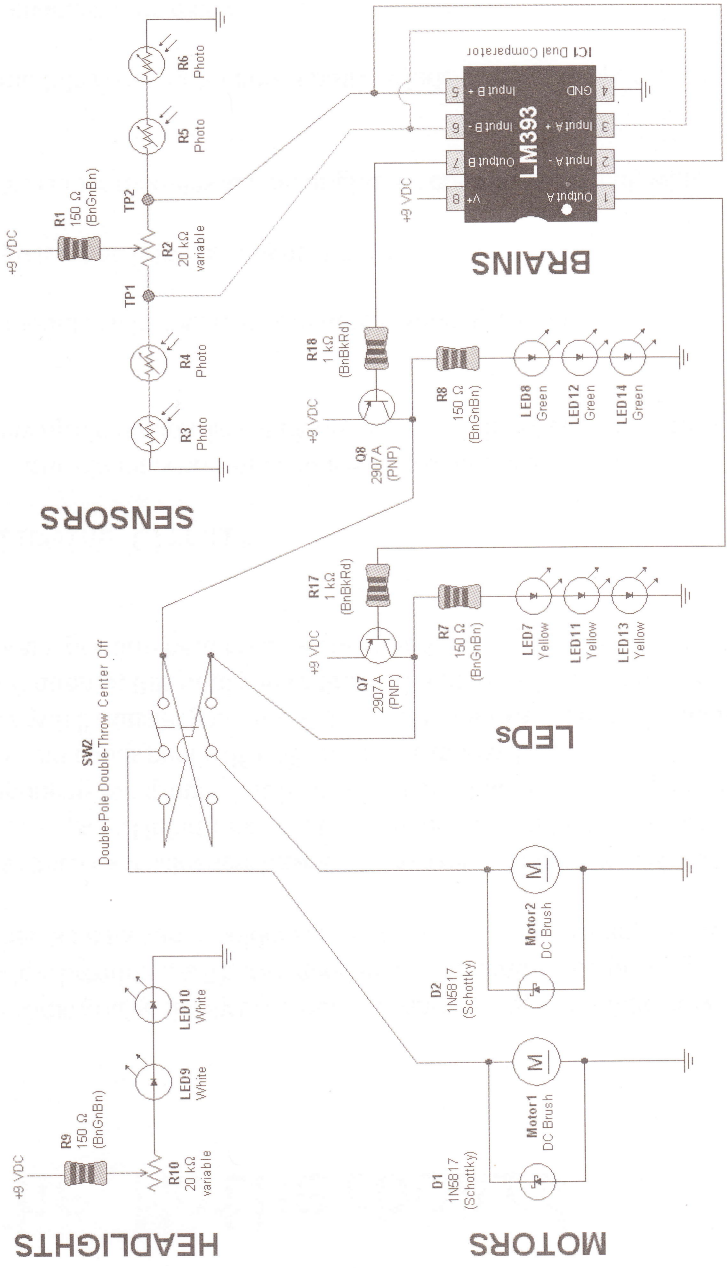


Figure 23-1. Wiring diagram of the final line-following circuit



HEADLIGHTS

MOTORS

LEDS

SENSORS