



**Complete Circuit:**

555 Timer provides PWM at 27Khz

$R_{sense} = .33\Omega @ 3W$  to provide

1.7-1.8Amps split between the two

LED Strings

LED Arrays are 10W emitters, Array 1

is Cool White, Array 2 is Warm White

Jules Ryckebusch May 2017