

Tweet 'n' Knock by F. Granelli  
Breadboard implementation

Resistors are: 10 kohm for diodes, 10 ohm for button, 1 Mohm for piezo

Ethernet shield is not drawn in the figure

