



## Arduino Dice


by [nick\\_rivera](#) on June 30, 2013

### Table of Contents

Arduino Dice .....	1
Intro: Arduino Dice .....	2
Step 1: Parts .....	2
Step 2: LEDs .....	3
Step 3: Connect LEDs to ground .....	3
Step 4: Jumpers to the arduino .....	4
Step 5: Pushbutton .....	4
Step 6: Connect the jumpers to the Arduino .....	5
Step 7: Code! .....	6
File Downloads .....	6
Related Instructables .....	6
Advertisements .....	7
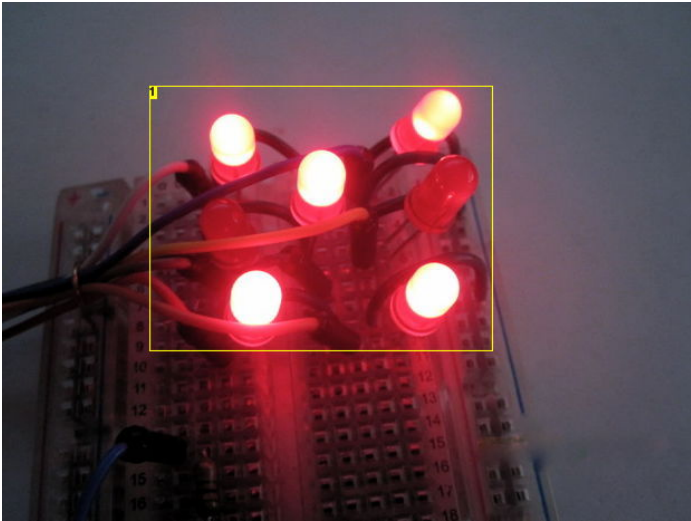
## Intro: Arduino Dice

This instructables will show you how to create electronic dice out of an Arduino and a few other components.



### Image Notes

1. Five!

## Step 1: Parts

What you will need:

18 Jumpers (11 large 7 small)

7 LEDs (I used red ones)

Pushbutton

Resistor (I used 100ohm, 10 ohm would work too)

Solderless breadboard

Arduino (+usb cable for connection)


Optional: small strapdown copper jumpers

Tools:

Wire cutters

Computer

Okay, lets build it.

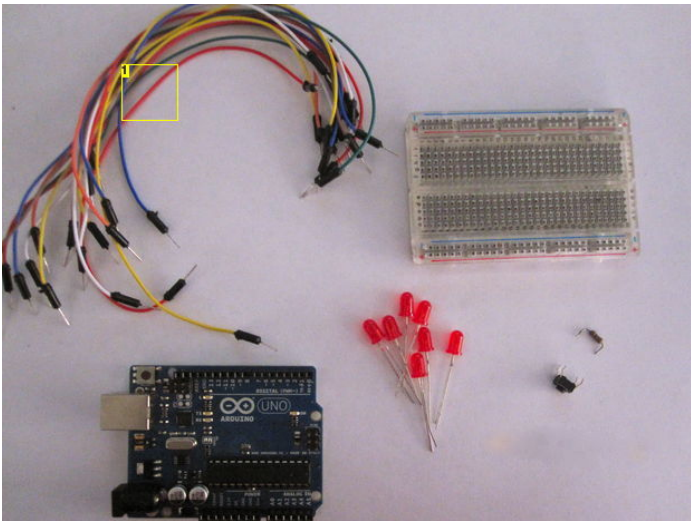



### Image Notes

1. Optional but recommended- some small jumper wires
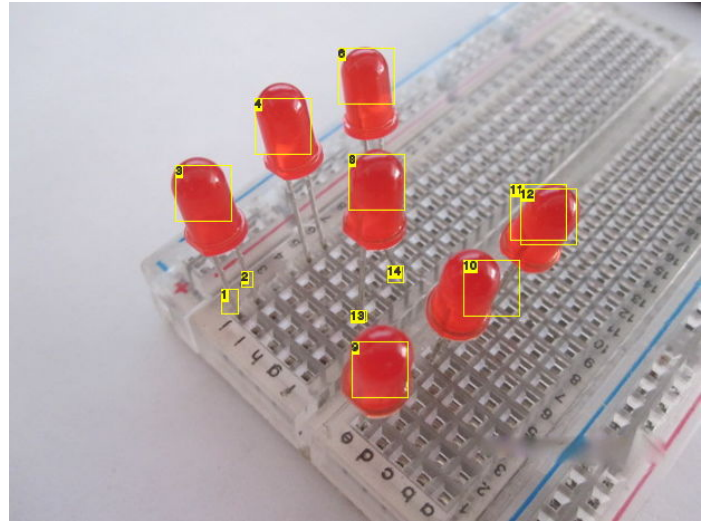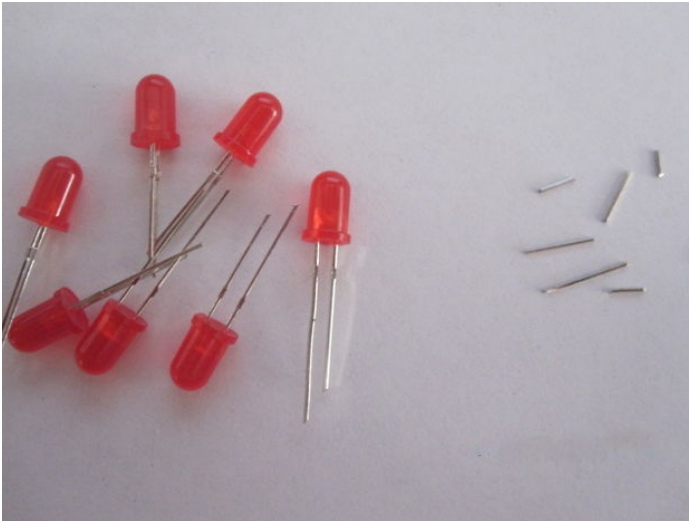
## Step 2: LEDs

First start by cutting the leds shorter, so they fit better on the breadboard.

Then start arranging them onto the board, having the negative side of the leds point to the left. LED 1 goes between pins (1-,2+) LED 2 goes on (5-,6+) and LED 3 on (9-,10+). LED 4, in the middle, must be stretched between (4-, 7+). The last 3 LEDs go directly below the first 3 leds, but on the other side of the breadboard.




### Image Notes

1. -negative
2. positive
3. LED1
4. LED2
5. LED3
6. LED3
7. LED4
8. LED4
9. LED5
10. LED6
11. LED7
12. LED7
13. Negative for LED4 on 4
14. Positive for LED4 on 7
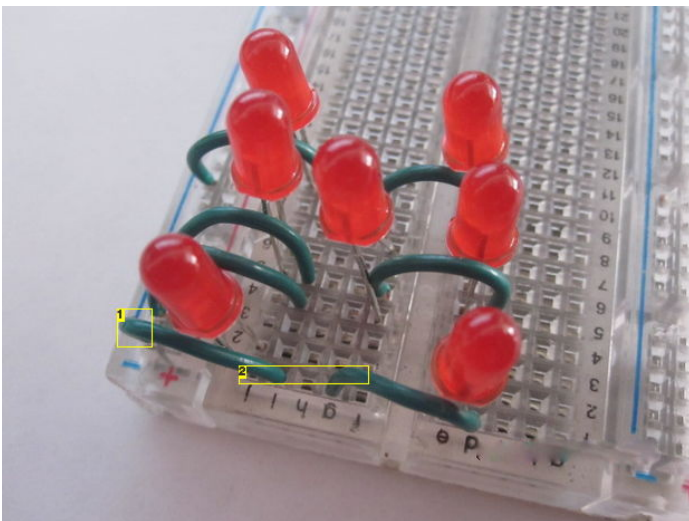
## Step 3: Connect LEDs to ground

Grab your jumpers (for this step I used the smaller jumpers to make life easier) and connect all of the negative(-) sides of the LEDs to the ground rail.




### Image Notes

1. All of the negative sides of the leds are connected to the ground rail
2. Optional- smaller jumpers make it easier to manage.
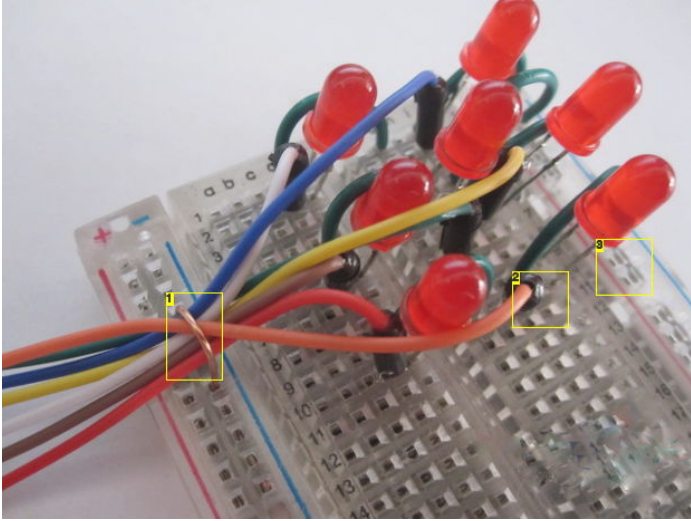
#### Step 4: Jumpers to the arduino

Now, get out your large jumpers, and put a jumper onto each positive(+) side of the leds. It is much easier if you color code the jumpers, it will help later. Also connect a large jumper to the ground rail, and that will connect to the ground on the arduino. In the list it was optional, but I used a small piece of coated copper wires to hold all the large jumpers down.




##### Image Notes

1. Used copper wire to hold all the jumpers into place
2. Each jumper connected to the ( ) side of the leds
3. Connect another jumper to the ground rail


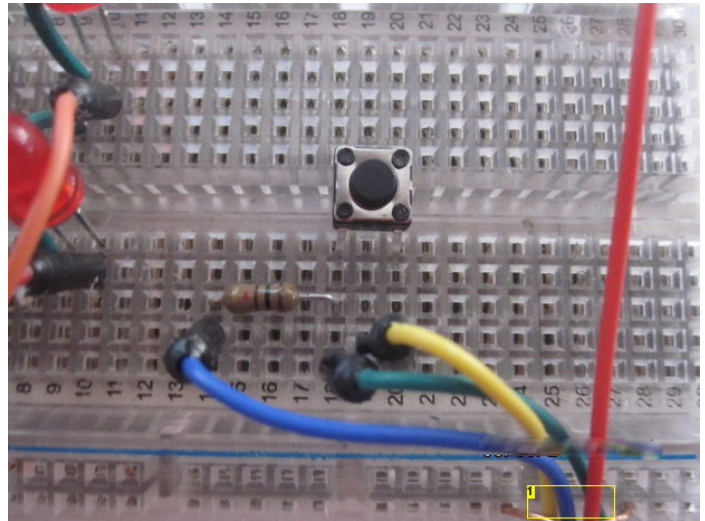
#### Step 5: Pushbutton

Now, we connect the pushbutton. Start by placing the pushbutton onto the board, between the crack in the board. I used a 100kohm resistor, but others would work too. Place said resistor onto the board coming off of one of the pushbutton sides (see the diagram for further understanding).



##### Image Notes

1. another copper tie-down  
:|  
its an ocd...

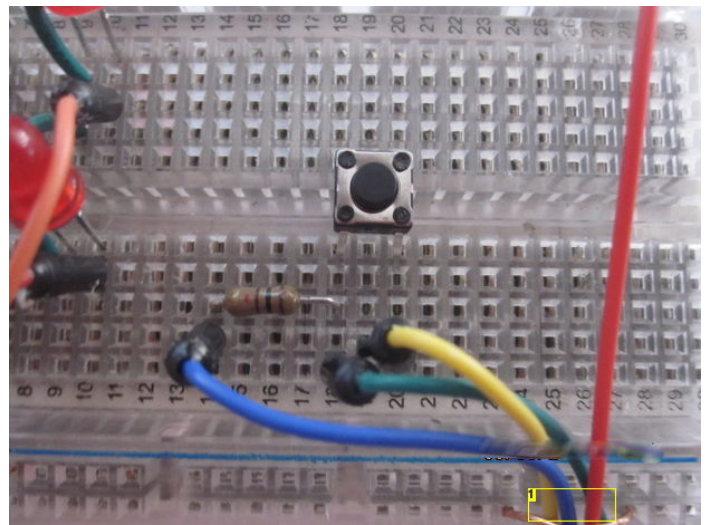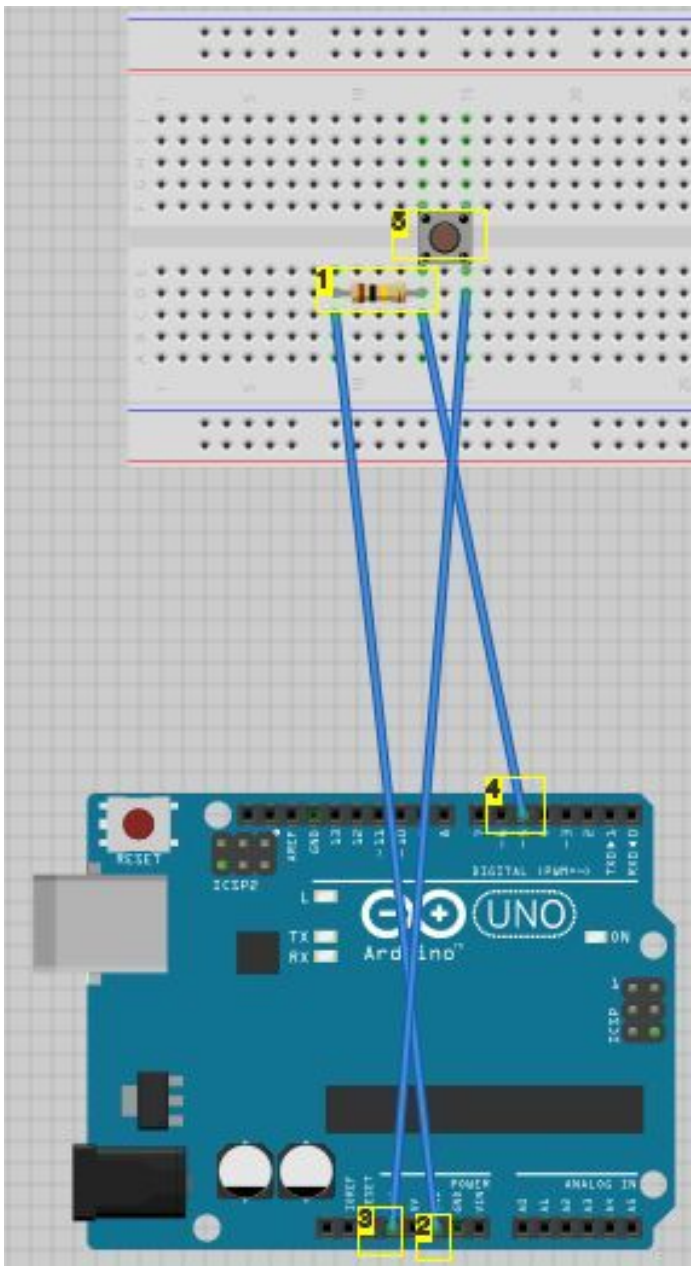

#### Image Notes


1. Said resistor
2. Connected to gnd
3. 3.3V on arduino
4. Pin ~5
5. Pushbutton

### Step 6: Connect the jumpers to the Arduino

Now, we connect the jumpers onto the arduino board itself.

- LED1/Pin 12
- LED2/Pin ~11
- LED3/Pin ~10
- LED4/Pin ~9
- LED5/Pin 8
- LED6/Pin 7
- LED7/Pin ~6
- GND/GND :o

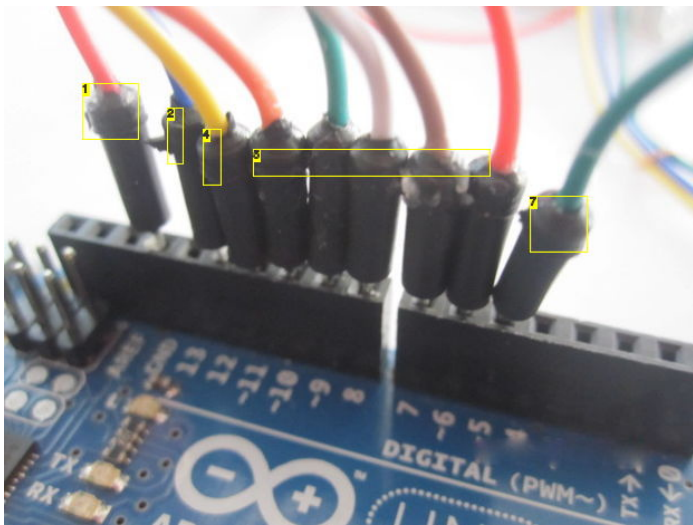If you did not already connect the pushbutton to the arduino board, the previous step shows that.




#### Image Notes

1. GND connected to the gnd rail on the breadboard
2. LED1/Pin 12
3. LED2/Pin ~11
4. LED2/Pin ~11
5. and so forth
6. Pushbutton
7. Pushbutton
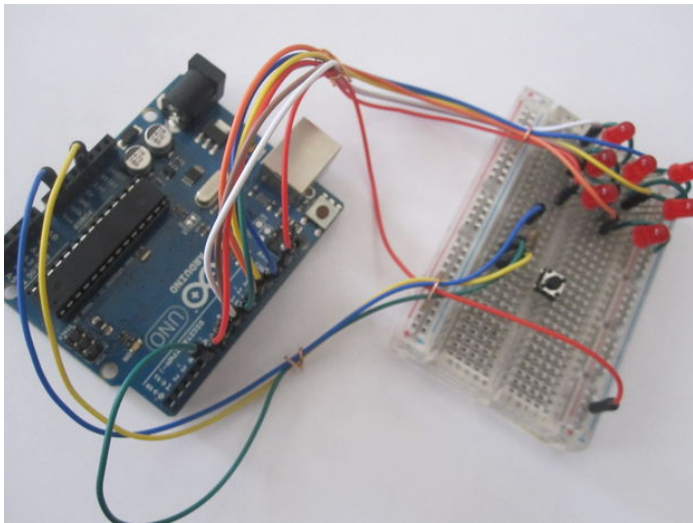
### Step 7: Code!

Now, connect the arduino board to your computer and upload this code.



#### File Downloads



**ArduinoDie.ino.zip** (670 bytes)

[NOTE: When saving, if you see .tmp as the file ext, rename it to 'ArduinoDie.ino.zip']

#### Related Instructables



**LED Die with Arduino** by braulio777



**TinyDice LED die (Arduino compatible)** (Photos) by emihackr97



**Led Dice** by agupta52



**Arduino Five Pin LED Matrix Dice** by simonfrfr



**Arduino: Electronic Dice (using random numbers)** by redryno1221



**ATtiny85/45/25 LED dice (Super simple and CHEAP!)** by xBacon

