

## Phantom Power Blocker (protect Your Dynamic Microphones)



by simpletronic


**Condenser microphones** contain internal circuitry and capsule which require a power supply. **Phantom power** uses the same wires of the mic balanced output signal to carry that energy from the **mixer console** to the **microphone**. Phantom power is required by condenser mics but not by dynamic (*moving coil*). Professional mixers give you the option to switch the the **phantom power** on or off for each input channel. Semi-pro and consumer mixers enable or disable the phantom voltage globally or in groups of input channels. In general, connecting a dynamic

mic to a phantom powered input is not a problem as both ends of the coil (*or transformer*) will be at the **same voltage** and no current will flow through them. This holds true as long as the connection is a correctly wired **balanced cable**. There are many other situations under which phantom power can cause damage to connected devices. This simple circuit **blocks** the phantom voltage to safely connect any device to a **48v** powered input channel.




---


### Step 1: Circuit Diagram

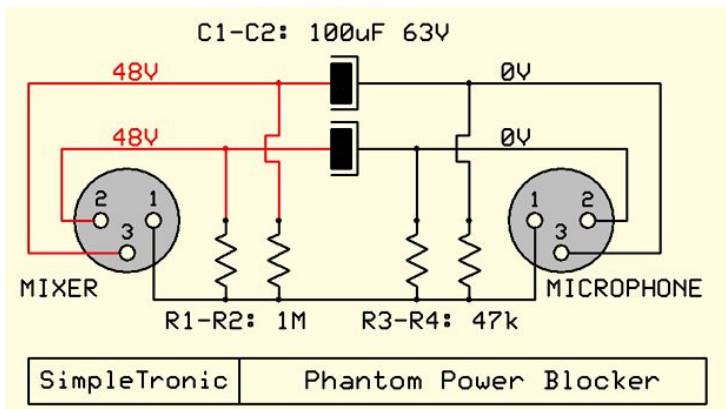


## Step 2: How It Works

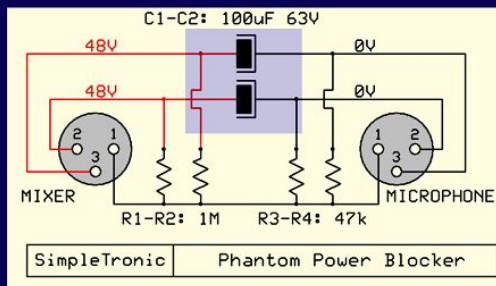

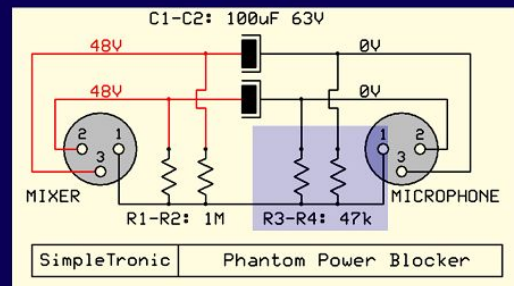Capacitors C1 & C2 block the 48V DC (or 24v/12v) phantom power from reaching the mic or device, and at the same time allow the passing of audio signal from mic to mixer.




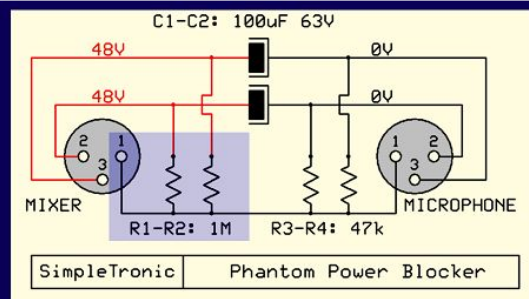R3 and R4 are necessary for the correct polarization of the electrolytic capacitors C1 & C2.








R1 and R2 are for discharging C1 & C2 when circuit is disconnected.
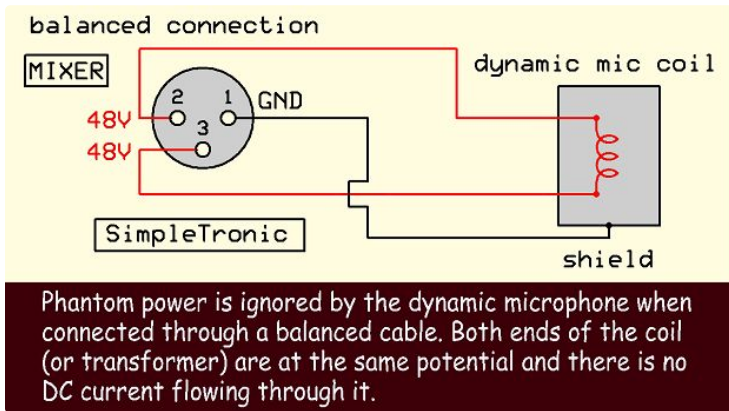
## Step 3: Connecting With Balanced Cable Is Safe


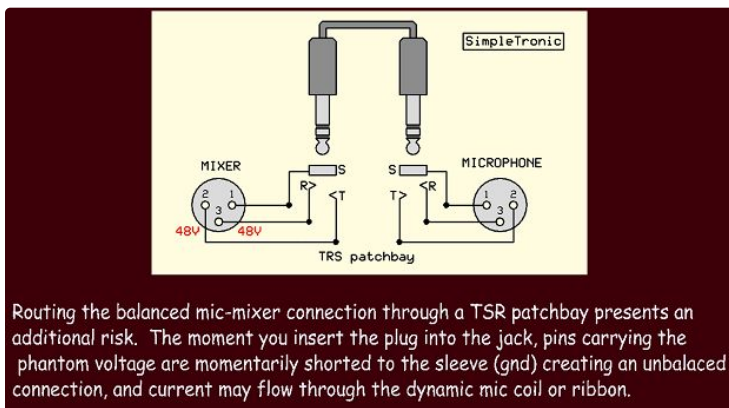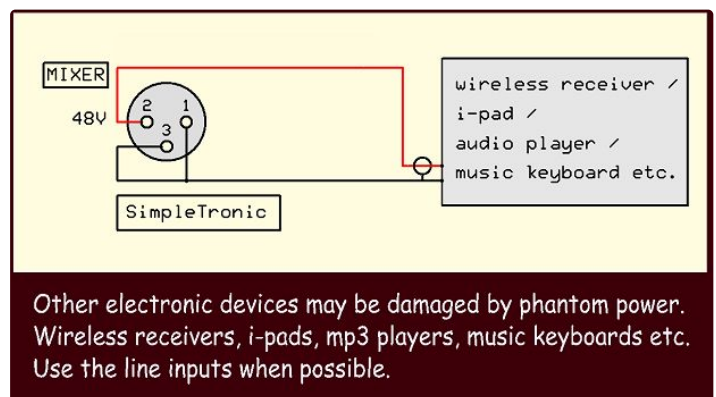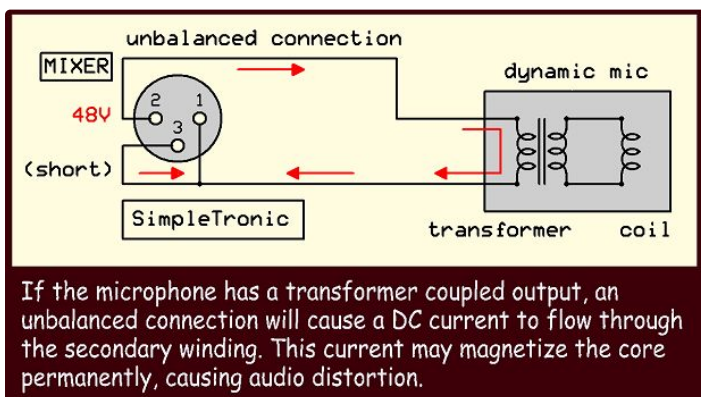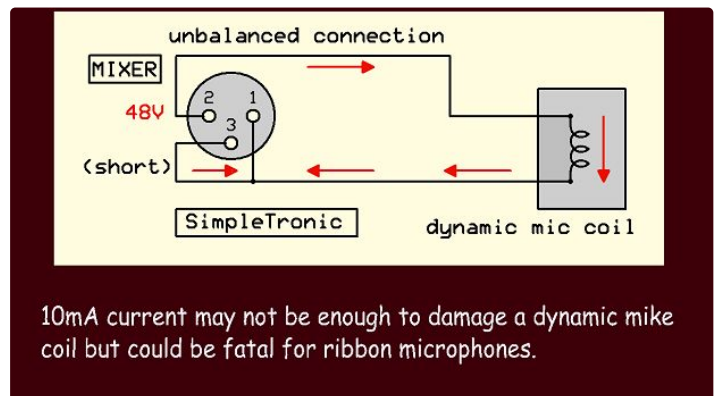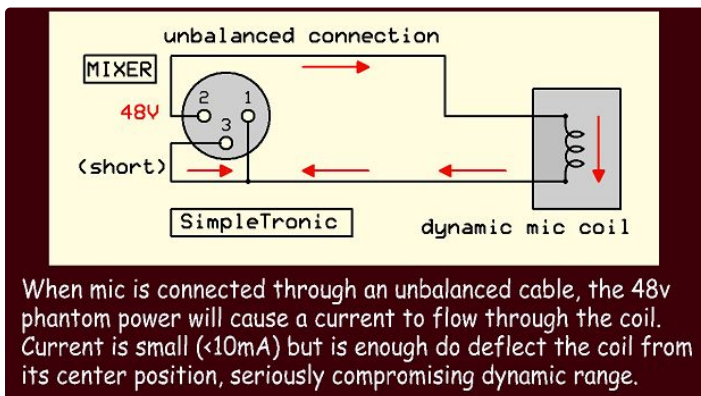
#### Step 4: These Configurations Are Not Safe for Dynamic / Ribbon Mics and Other Devices.



---

## Step 5: Watch the Video! Thank You

<https://youtu.be/ufZs-9WAIDk>



Thanks for the information. I also need to add a muting feature to this circuit.